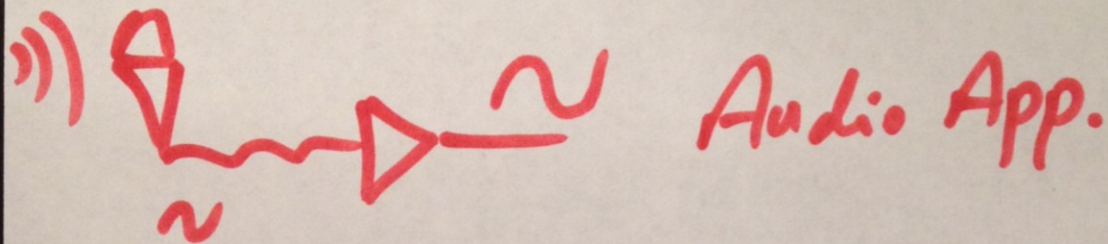


The Signal Path Blog

<http://www.TheSignalPath.com>

**Tutorial on the Theory, Design and Characterization of a
Single Transistor Bipolar Amplifier**

Amplifier Design:



Specification:

$$\text{Gain} = 100 \text{ V/V}$$

$$\text{BW} > 20 \text{ kHz}$$

$$\text{Supply} = \pm 2.5 \text{ V}$$

$$\text{Power} < 50 \text{ mW}$$


Common Emitter:

NPN Device: $\beta \approx 100$

$$V_{BE} \approx 0.6V$$

Assume: $\beta \approx \beta + 1$, $V_{CESAT} = 0.2V$


$$I_C \approx I_E$$

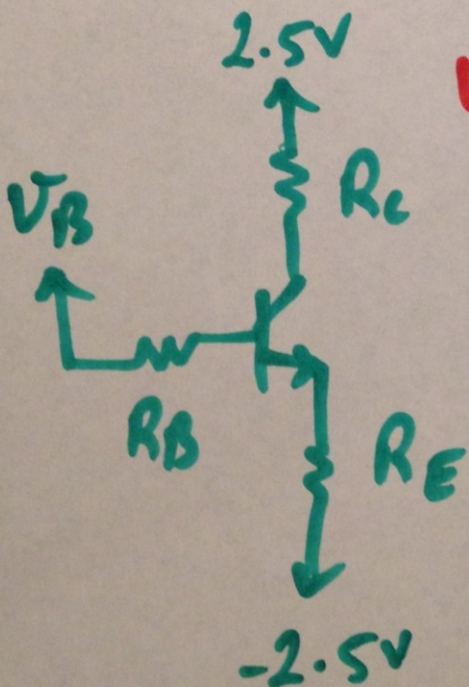

$$V_B - I_B R_B - V_{BE} - I_E R_E = -2.5V$$

$$I_E = \frac{V_B + 2.5 - V_{BE}}{\frac{R_B}{\beta} + R_E}$$

Signal Swing

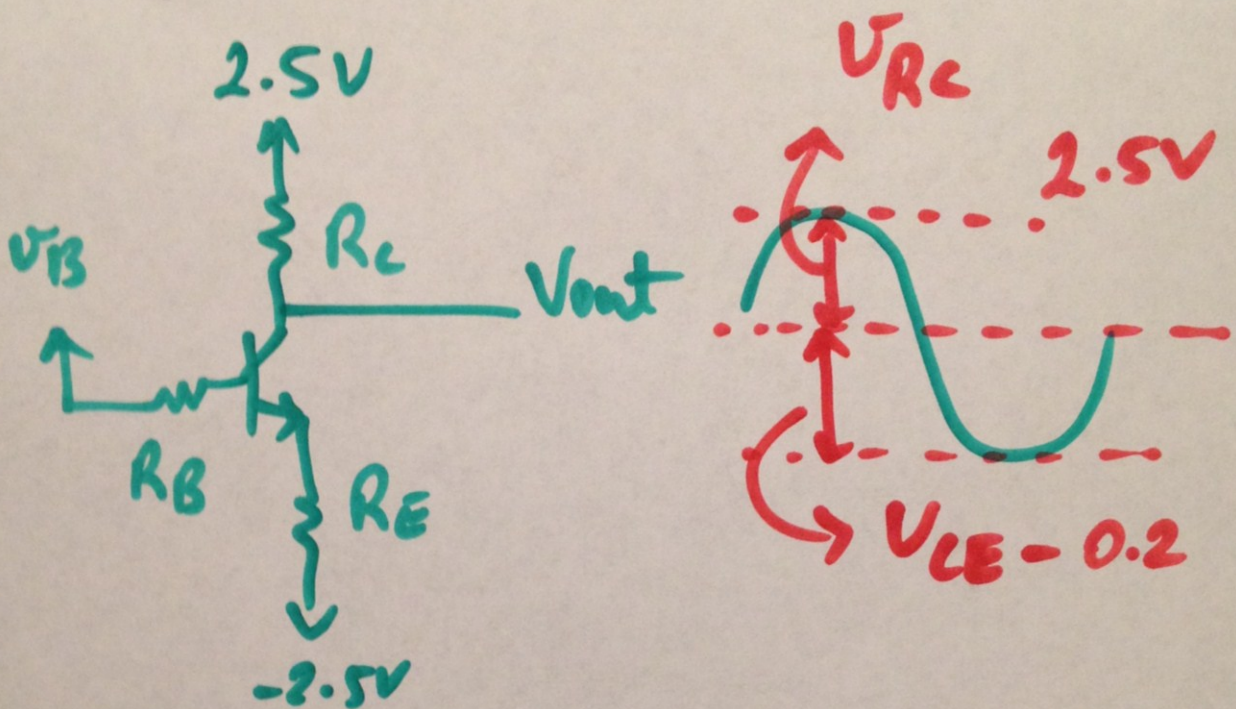

$$\text{Positive Swing} = V_{RC}$$

$$\text{Negative Swing} = V_{CE} - 0.2$$

↑
 V_{CE-SAT}

Maximize:


$$V_{RC} = (V_{CE} - V_{CE-SAT}) = V_{RE}$$

$$V_{RC} + V_{CE} + V_{RE} = 5V$$

$$\therefore \begin{cases} V_{CE} = 1.8V \\ V_{RE} = 1.8V \\ V_{RC} = 1.8V \end{cases} \quad \textcircled{1}$$

$$\therefore R_C = R_E$$


Small Signal:

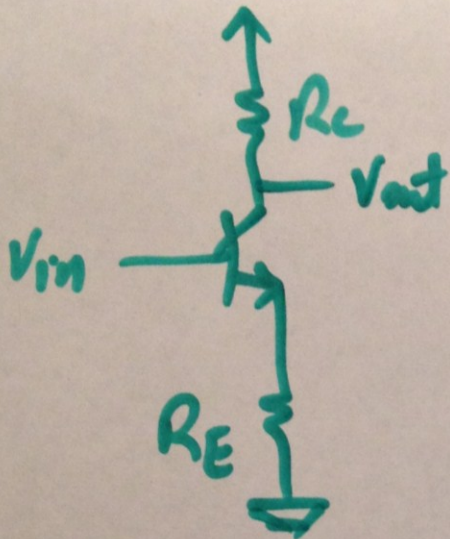

$$\frac{V_{out}}{V_{in}} = ?$$
$$= \frac{-g_m}{1 + g_m R_E} \cdot R_C \approx$$

$$-\frac{R_C}{R_E} \approx -1 \text{ V/V}$$


Add Cap:

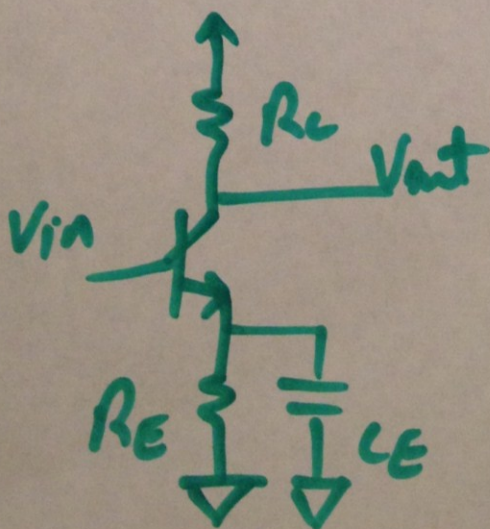

$$A_v = -g_m R_C$$

$$= \frac{-I_C}{V_T} \cdot R_C$$

$$= (1.6)(40) = -64 \text{ [V/V]}$$

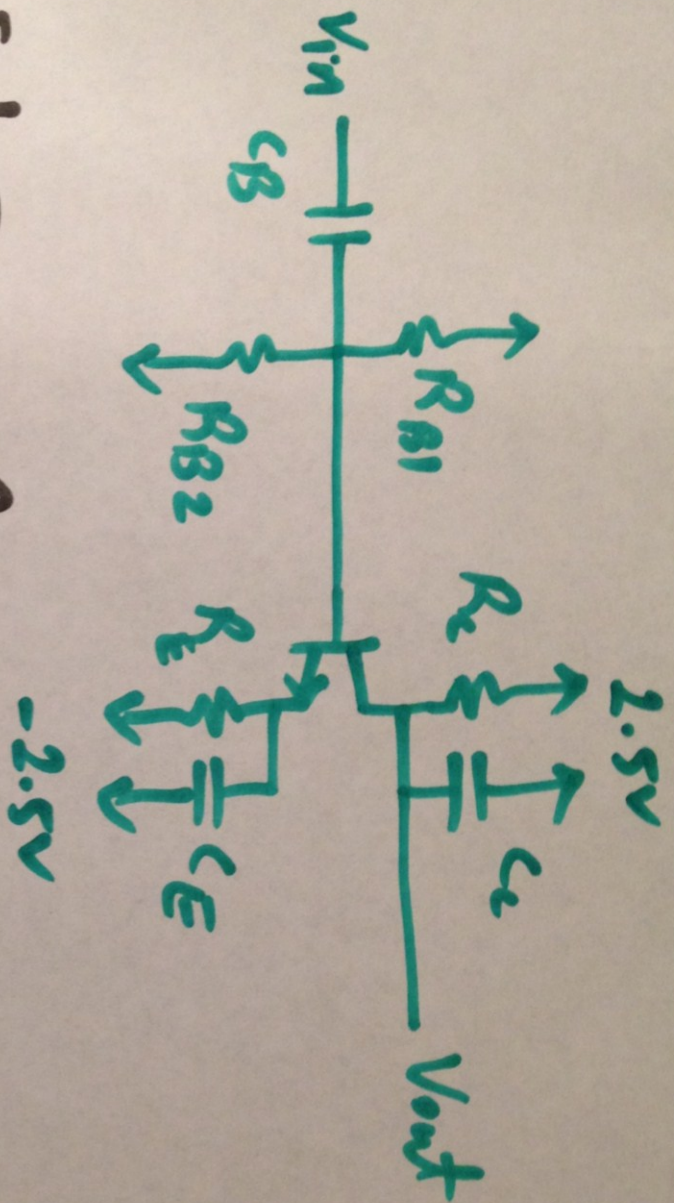


Set $I_C = 2\text{mA}$

$$\Rightarrow R_C = R_E = 800\Omega$$

$$\Rightarrow R_{B1} = \text{~~14k}\Omega~~ \quad 14\text{k}\Omega, \quad R_{B2} = 10\text{k}\Omega$$

$$\Rightarrow C_C = 10\text{nF} \Rightarrow \text{BW} \approx 20\text{kHz}$$

Two Stage Amp:

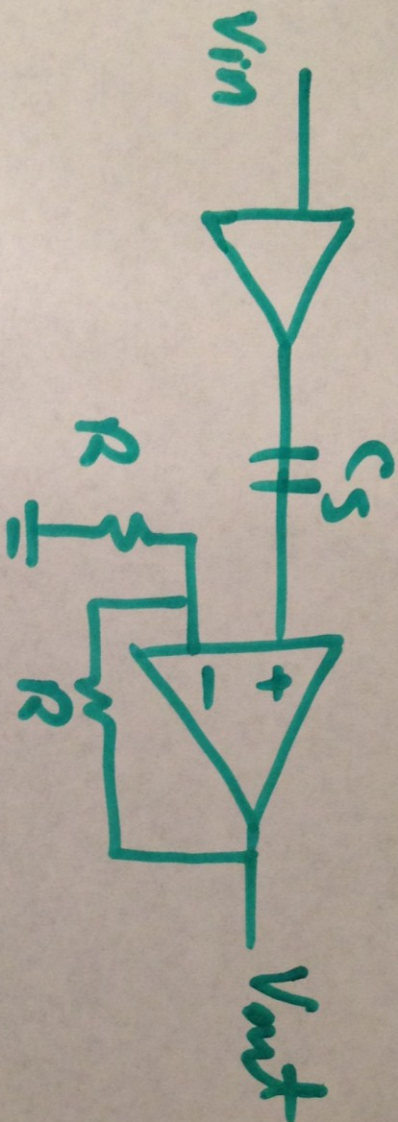

$$A = 1 + \frac{R}{R} = 2 \text{ V/V}$$